
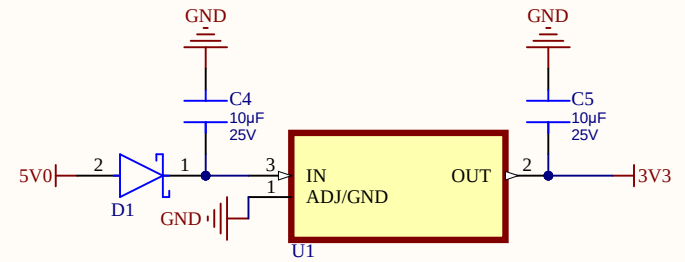


Now here is the main STM32F103C8T6 chip where it forwards the i2c communication from the INA228 to the lcd to be displayed

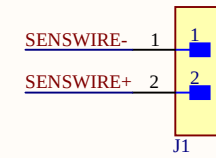
Here is the voltage regulator outputting a clean 3.3V signal




These are the 2 sensing probes




This is for the LCD display

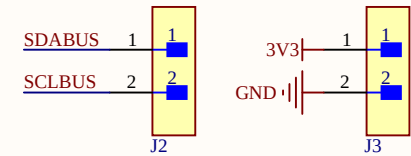


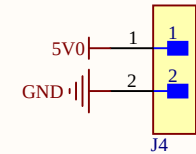
This is where the power source connects to



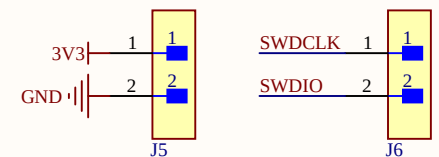These headers are for the SWD Programmer to program the chip



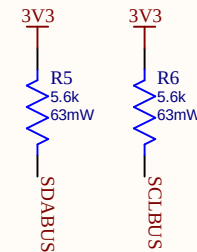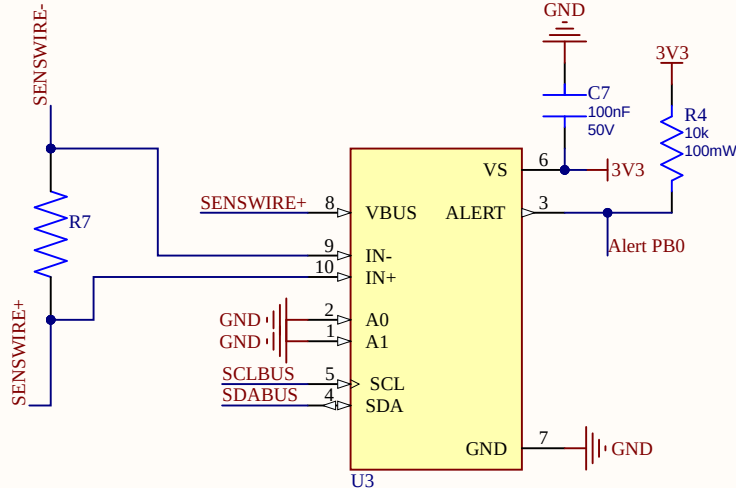Here is the INA228AIDGSR IC that measure the current and coms through I2c



Title		
Size	Number	Revision
A		
Date:	6/25/2026	Sheet of
File:	C:\Users\...\curr_sens_sch.SchDoc	Drawn By:

Board Stack Report